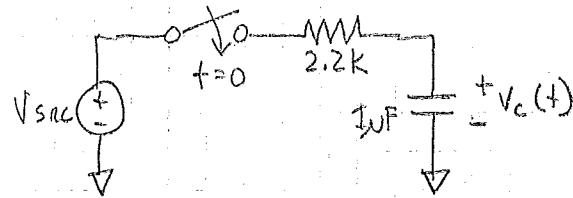


2. For the circuit below, At what time will  $V_c(t)$  reach 99% of  $V_{SRC}$ ?



$$V_c(t) = V_{SRC} \left(1 - e^{-t/RC}\right)$$

rephrasing the question now, is ...

At what time does  $(1 - e^{-t/RC}) = 0.99$

$$0.99 = 1 - e^{-t/(2.2 \times 10^3)(1 \times 10^{-6})}$$

$$0.01 = -e^{-t/(2.2 \times 10^3)}$$

$$-4.61 = -t/(2.2 \times 10^3)$$

$$\underline{\underline{t = 10.1 \text{ ms}}}$$

This result validates the rule-of-thumb that tells us that after  $10T$ ,  $V_c$  is essentially equal to  $V_{SRC}$ .