


RCL Problems

EECE 1010

16.1.16.27

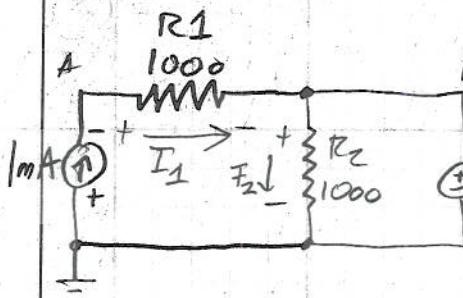Problem Q - (2pts)

Use the Node Method to find power dissipated by the 1mA current source.



$$B = 1V$$

$$\text{Node A: } 1\text{mA} - I_1 = 0$$

$$I_1 = 1\text{mA}$$

$$I_1 = \frac{V_a - 1}{1000}$$

$$1\text{mA} = \frac{V_a - 1}{1000}$$

$$1 = V_a - 1$$

$$2 = V_a$$

$$P_{diss} = V \cdot I$$

$$V = V_{\text{positive}} - V_{\text{negative}}$$

$$V = 0 - 2V$$

$$V = -2V$$

$$P_{diss, 1\text{mA}} = -2V (1\text{mA}) = -2\text{mW}$$

$$P_{diss, 1\text{mA}} = -2\text{mW} \quad | \quad (2\text{pts})$$

$$\text{Note: } I_p = \emptyset \text{ A}$$