


KVL

11. For the circuit below, find the following:

1. VR_3

2. I_x

3. Power dissipated by V_2

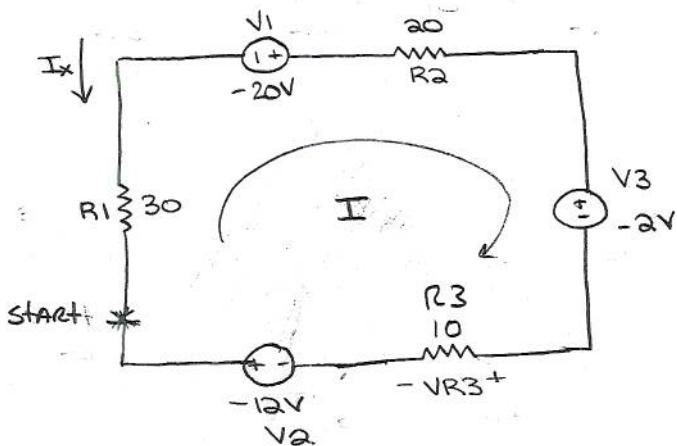

Conceptually easier to think
of I going clockwise

Choosing I clockwise to directly compute VR_3
Note: I will be $(-1) * I_x$

$$30I - (-20) + 20I - 2 + 10I - (-12) = 0$$

$$30I + 20 + 20I - 2 + 10I + 12 = 0$$

$$60I = -30$$

$$I = -0.5 \text{ , thus } VR_3 = -5 \text{ volts}$$

$$I_x = 0.5A$$

$$P_{V2} = IV$$

@ V_2 :

$$P_{V2(\text{Diss})} = -6W(\text{diss})$$