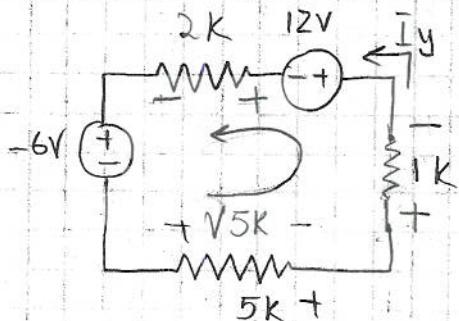


#13 (6 pts) Determine I_y , V_{5k} , and power generated by -6V Source.



$$\sum V \text{ across branches} = 0$$

$$V_{5k} + V_{1k} + 12 + V_{2k} + (-6v) = 0$$

$$I_y \times 5k + I_y \cdot 1k + 12 + I_y \cdot 2k - 6v = 0$$

$$I_y (5k\Omega + 1k\Omega + 2k\Omega) = -6 \text{ Volts}$$

$$I_y = \frac{-6 \text{ Volts}}{8k\Omega} = -.75 \text{ mA}$$

$$\boxed{I_y = -.75 \text{ mA}} \quad (2 \text{ pts})$$

$$V_{5k} = I_y \times 5k\Omega = -.75 \text{ mA} \times 5k\Omega = -3.75 \text{ Volts}$$

$$\boxed{V_{5k} = -3.75 \text{ Volts}} \quad (2 \text{ pts})$$



$$P = I_y \times (-6v) = (-.75 \text{ mA}) (-6 \text{ Volts}) = 4.5 \text{ mW}$$

$$\boxed{P = 4.5 \text{ mW}} \quad (2 \text{ pts})$$