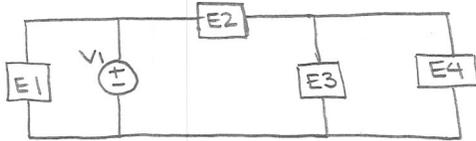


## (4pts) Problem 28

A schematic diagram is shown below with a voltage source and three unknown circuit elements in  $E_1$ ,  $E_2$ ,  $E_3$  and  $E_4$ . Circle the correct answer for the questions below.



- a) The voltage across  $E_3$  \_\_\_\_\_ the voltage across  $E_4$ .
- 1) is the same as
  - 2) is different from
  - 3) is unrelated to
- b) The current through  $E_3$  \_\_\_\_\_ the current through  $E_4$ .
- 1) is the same as
  - 2) is different from
  - 3) maybe unrelated to
- c) The current through  $E_2$  is equal to the current through  $E_3$  plus the current through  $E_4$ .
- 1) true
  - 2) false
  - 3) can't tell
- d) The voltage across  $V_1$  is equal to the sum of the voltages across  $E_2$  and  $E_3$  or  $E_4$ .
- 1) true
  - 2) false
  - 3) can't tell

For b.... If  $E_2$  was a voltage source, the voltage across  $E_3 + E_4$  would be the same regardless of their individual resistances and the current through one of them could not affect the other one. In that case, there is no relationship between the currents through  $E_3 + E_4$ .