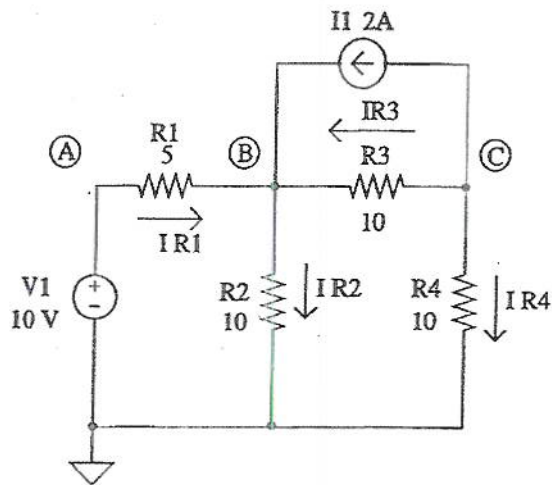


2. Write the SPICE netlist for the following circuit. Do NOT include .options etc. Write the netlist so that the indicated currents are correctly calculated. Include all reference designators.



V1	A	$\emptyset$	10
R1	A	B	5
R2	B	$\emptyset$	10
I1	C	B	2
R3	C	B	10
R4	C	$\emptyset$	10