

30

Consider the circuit below. Assume β for $Q_1 + Q_2$ is 100. If $I_{B2} = 930 \mu A$, what is the LED current and is Q_1 on or off. Assume $V_{LED(on)} = 2V$, $V_{CE(sat)} = 0.2V$

