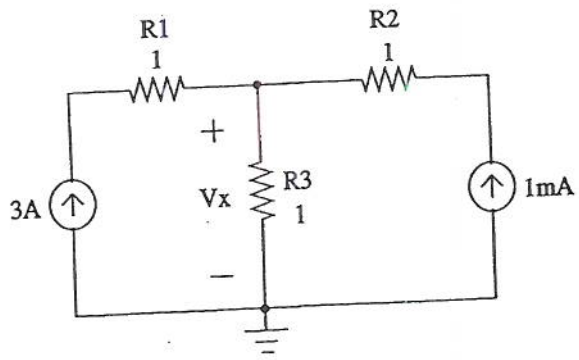


15. Use any method to find  $V_x$



Ans:  $V_x = 3.001V$