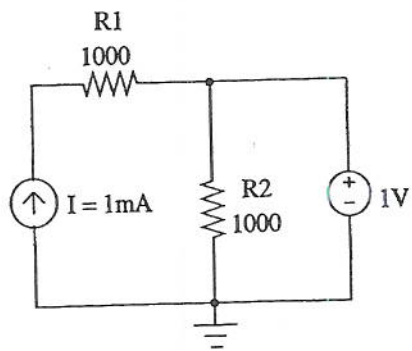


9. Use the node method to find power dissipated by the 1mA current source:



ANS: $P_{1mA} = -2mW$