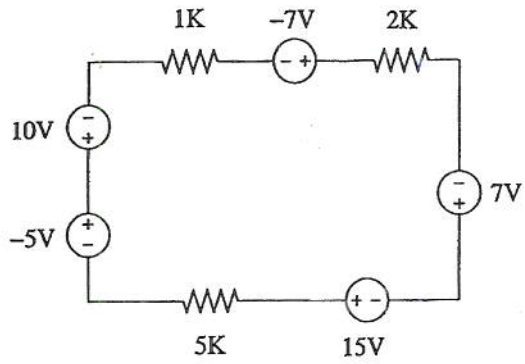


8. Draw an equivalent circuit that contains only one resistor and one voltage source. Solve for the current flowing in the loop of the equivalent circuit.



Ans:  $I=0$