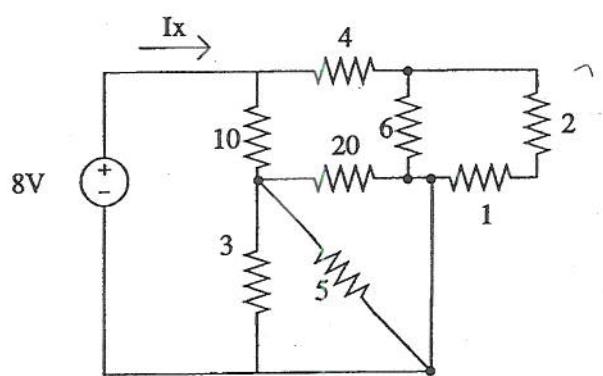


4. Determine the current I_x for the following circuit. Show your transformation of the resistor network.



$$I_x = 2.016 \text{ A}$$