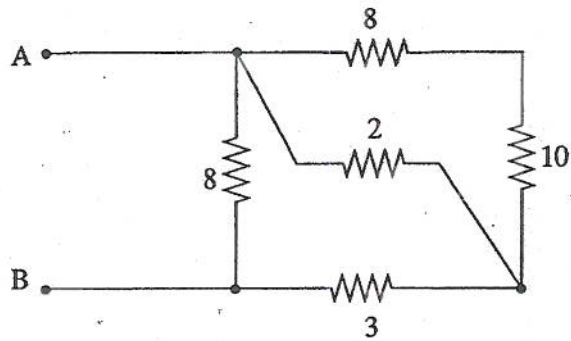


5. Determine the equivalent resistance between terminals A and B. Show each transformation step.



$$R_{eq} = 3\Omega$$