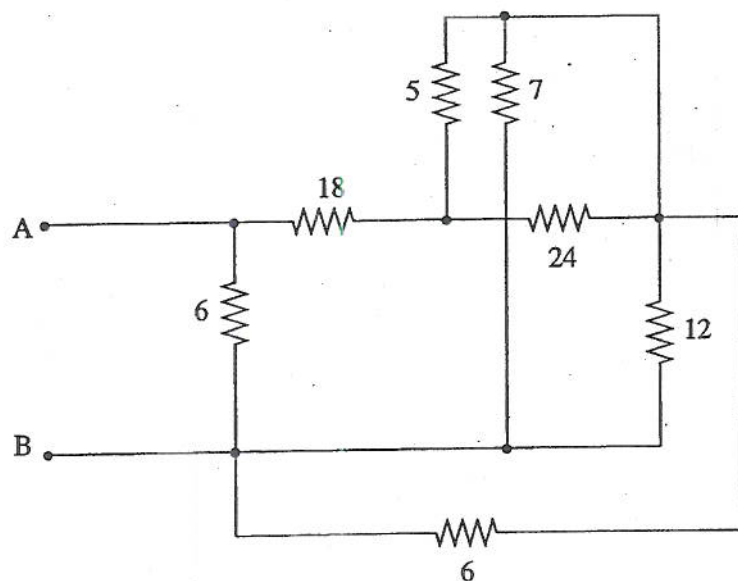


8. Determine the resistance between nodes A and B. Show all transformations.



$$R_{eq\ AB} = 4.83\ \Omega$$