

1. Calculate the power dissipated or generated by each source in the following circuits.

