

13. Fill in the blanks:

a) To disturb a circuit under test the least, an ammeter should have _____ internal resistance.

b) To disturb a circuit under test the least, a voltmeter should have _____ internal resistance.