

14. Draw a VI curve of:

a. A voltage source

b. A current source

c. A resistor