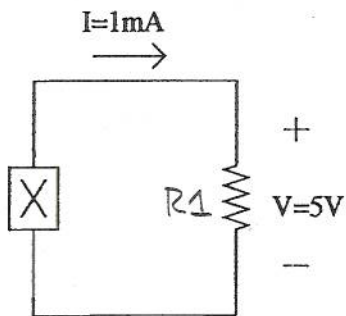


15. In the circuit below, R1 is connected to another circuit element, and has voltage and current as shown:



- a. From the information given, circuit element X is:
1. A voltage source
 2. A current source
 3. Can't tell
- b. The size of resistor R1 is _____.
- c. The power dissipated in R1 is _____.