
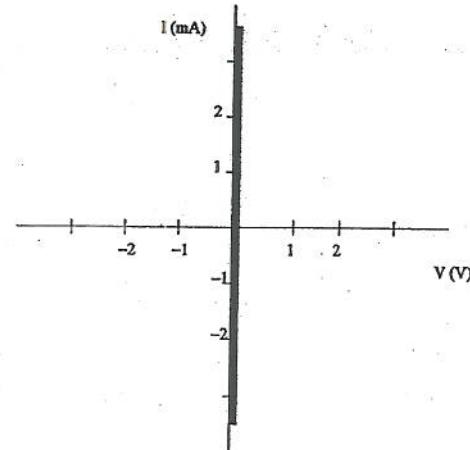


16. Match each of the following with the correct current-voltage (IV) plot, by writing the appropriate letter in the space by each plot.

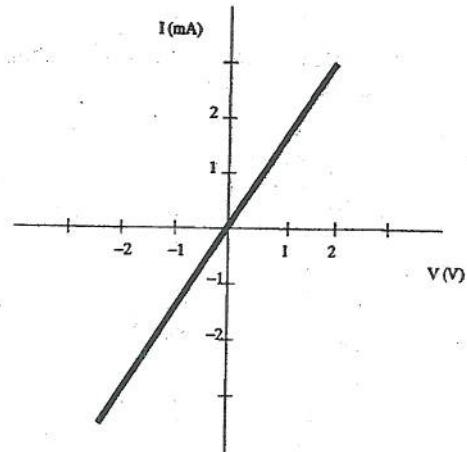
- a. Ideal voltage source (10V)
- b. Ideal current source (2mA).
- c. Open circuit
- d. Short circuit
- e. 2K Ohm resistor
- f. 500 Ohm resistor




1. _____




2. _____

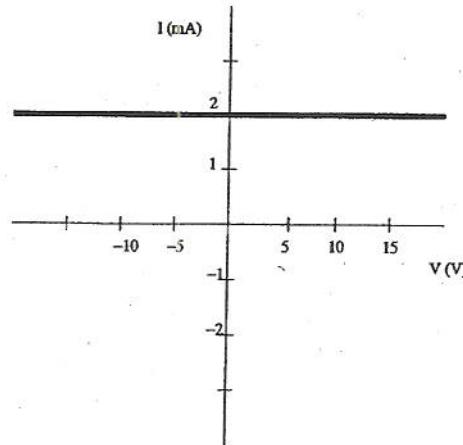


3. _____

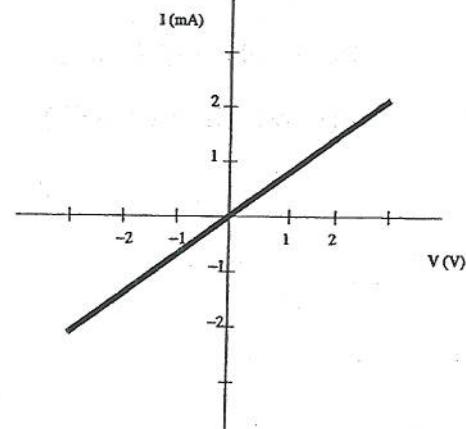

4. _____

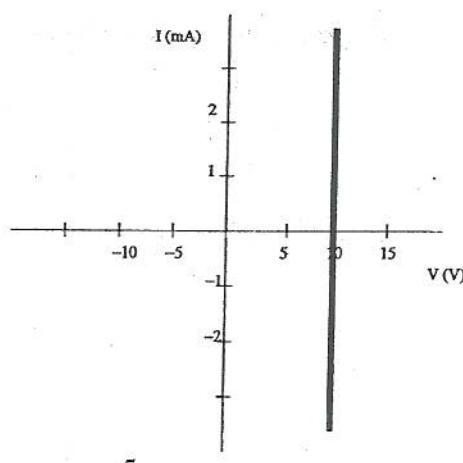

5. _____

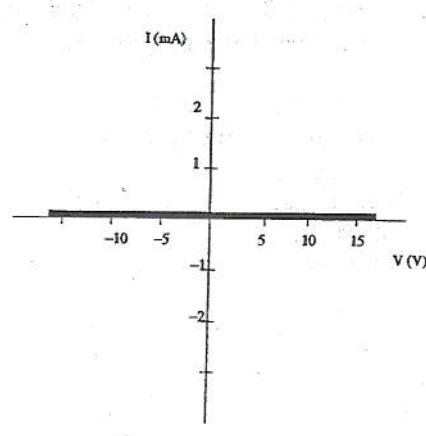

6. _____