

17. Use Ohm's Law to find I_1 :

