

2. Write the SPICE netlist for the following circuit. Do NOT include .options etc. Write the netlist so that the indicated currents are correctly calculated. Include all reference designators.

