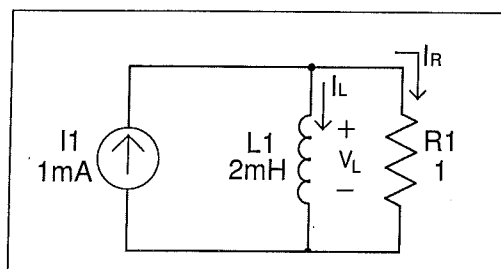


Inductors

4. The circuit below had been energized since before dinosaurs roamed the earth. At some later point in time however, a 50-ton titanosaur *Argentinosaurus huinculensis* steps on the 2mA current source, instantaneously removing it from the circuit at time $t = 0$.

- What is the value of I_L at time t_{0-} ? (t_{0-} is 'just before the current source gets stepped on.')
- What is the value of I_R at time t_{0-} ?
- What is the value of V_L at time t_{0-} ?
- What is the value of I_L at time t_{0+} ? (current source has 'just been removed')
- What is the value of I_R at time t_{0+} ?
- What is the value of V_L at time t_{0+} ?
- What is the value of I_L at time $t = \infty$?
- What is the value of I_{R1} at time $t = \infty$?



- I_L @ $t=t_{0-}$ is 1mA. All the current is flowing through the DC short circuit provided by L1.
- I_R @ $t=t_{0-}$ is zero. See (a)
- Since L1 is a DC short circuit, $V_L = 0$
- Since current cannot change instantaneously through L1, At $t=t_{0+}$ it continues to flow through L1 as before. (1mA)
- I_R @ t_{0+} will be -1mA. Current flows out of bottom of L1 and into bottom of R1.
- @ $t=t_{0+}$, $V_L = V_{R1} = -0.001V$. See (e)
- @ $t = \infty$, the inductor will have dissipated all its stored energy in R1, thus $I_L = 0$ @ $t = \infty$.
- I_{R1} @ $t = \infty$ will be zero. see (g)