

17. A lossless, $Z_o = 50\Omega$ transmission line is 1.0×10^6 meters long with $\epsilon_r = 1$. Its far end is shorted. At $t = 0$, an ohmmeter is connected to the near end. **Give the ohmmeter readings** at each time below. You may assume that the ohmmeter applies a voltage to measure resistance.

- (a) at time t_{0-} , ohmmeter reads: $\infty \Omega$, probes are not yet connected to the line
- (b) at time t_{0+} , ohmmeter reads: 50Ω , the incident wave is just starting down the line
- (c) at time $t = 2t_{d+}$, ohmmeter reads: 0Ω , after the reflected wave arrives, the short is apparent
- (d) at time $t = \infty$, ohmmeter reads: 0Ω