

- (a) Determine the delay times t_{r1} of line 1 and t_{r2} of line 2.

$$t_{r1} = 2.5 \text{ nS}$$

$$\underline{t_{r2} = 5 \text{ nS}}$$

- (b) Determine the generator resistance R_G .

$$b = 12 \left(\frac{50}{50 + R_g} \right) \quad R_g = \underline{\underline{50 \Omega}}$$

- (c) Determine the reflection coefficient ρ_{11} at the junction between the two lines.


$$\begin{array}{c} \overline{50\Omega} \quad | \\ \overline{} \quad | \\ \overline{100} \end{array}$$

$$\Rightarrow \rho_{11} = \frac{100 - 50}{150} = \underline{\underline{\frac{1}{3}}}$$

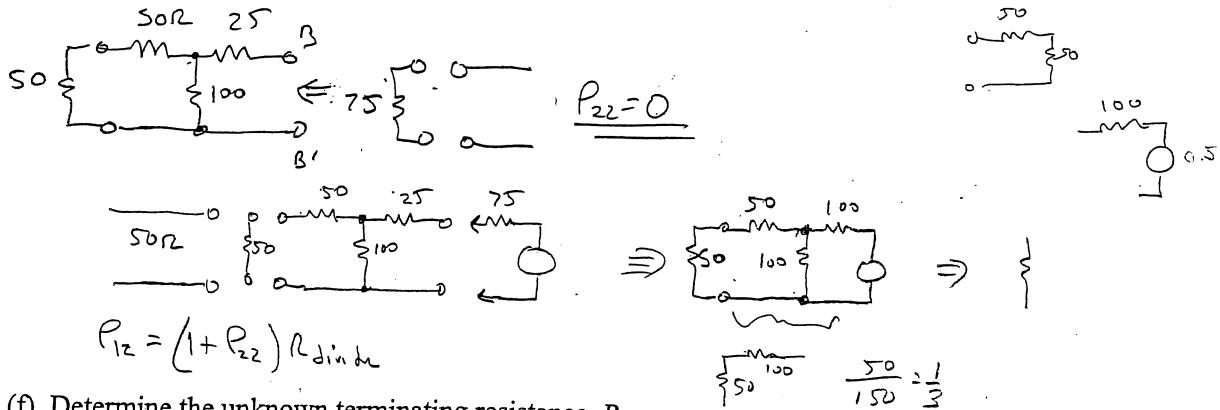- (d) Determine the transmission coefficient ρ_{21} at the junction between the two lines.

$$\text{from graph; } \rho_{21} = \frac{V_{B3}}{V_{A1}} = \frac{3V}{6V} \frac{4\Omega}{1\Omega} = 0.5$$

- 13
- (e) Determine the reflection coefficient ρ_{22} and the transmission coefficient ρ_{12} at the junction between the two lines.



- (f) Determine the unknown terminating resistance R_L .

V_{BB} sees positive reflection of 2V

$$\rho_L = \frac{2}{3} = 0.667$$

$$0.667 = \frac{R_L - 75}{R_L + 75} \Rightarrow R_L = 375 \Omega$$

Also, reflection from SMPL is
2V, incident was 3 so $\rho_L = 0.667$

- (g) Determine the steady-state voltages (i.e. for $t \rightarrow \infty$) at the input of the first line (A-A') and at the input of the second line (B-B').

