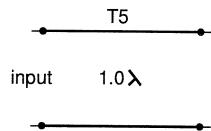
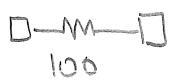
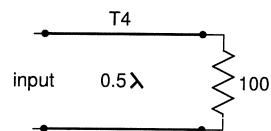
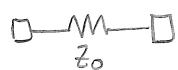
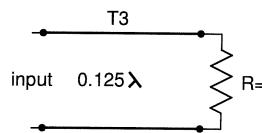
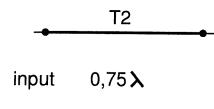


3. The electrical length of several transmission lines are given below. At a frequency corresponding to  $\lambda$  :
- draw the equivalent lumped circuit the line would present at its input terminals
  - give the impedance at the input of the line



(b)

Short circuit ( $\frac{1}{2}$  line replicates  $10\Omega$ )  
Impedance at the input

short circuit (equiv to  $\frac{1}{4}$  line)

$Z_0$  (Any line terminating in its  $Z_0$  has)  
 $Z_{in} = Z_0$

$100\Omega$  ( $\frac{1}{2}$  lines replicate their loss)  
Impedance at the input

open circuit ( $\frac{1}{2}$  multiples replicate the)  
end point impedance