
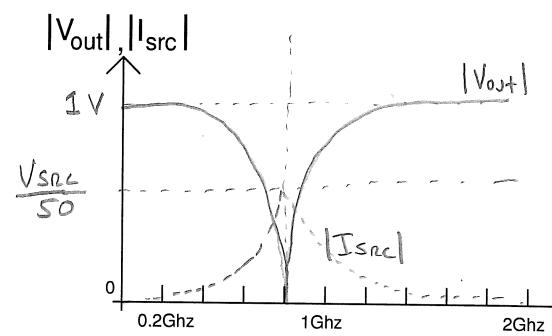


5. For the circuit below, draw  $|V_{out}|$  and the current  $|I_{src}|$  for frequencies from 0 to 2 Ghz. Use the same vertical axis for voltage and current. The resonant frequency is found at:  $f_0 = \frac{1}{2\pi\sqrt{LC}}$

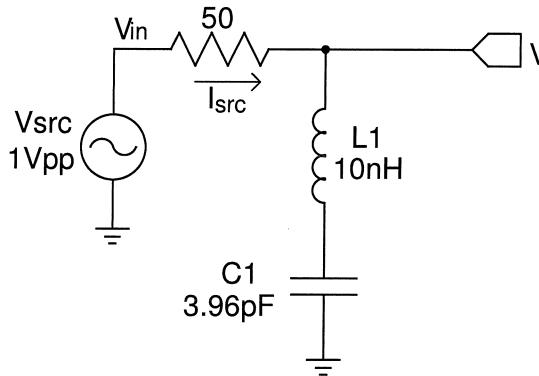

Resonant frequency of series network is  $f_0 = \frac{1}{2\pi\sqrt{LC}}$

$$f_0 = \frac{1}{2\pi\sqrt{(10 \times 10^{-9})(3.96 \times 10^{-12})}} \approx 800 \text{ MHz}$$

Series network  $Z_{in}=0$  at resonance so at 800 MHz  $V_{out} \rightarrow 0$

$$\text{At } 800 \text{ MHz } I_{src} = \frac{V_{src}}{50}$$