
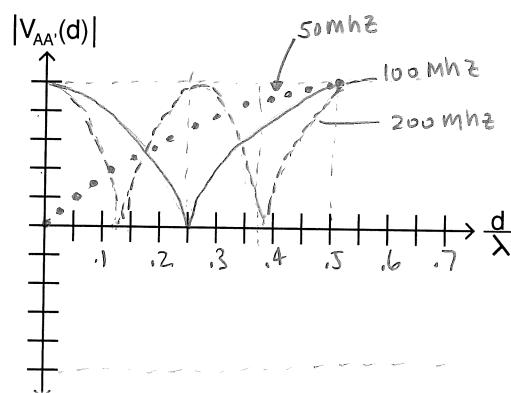
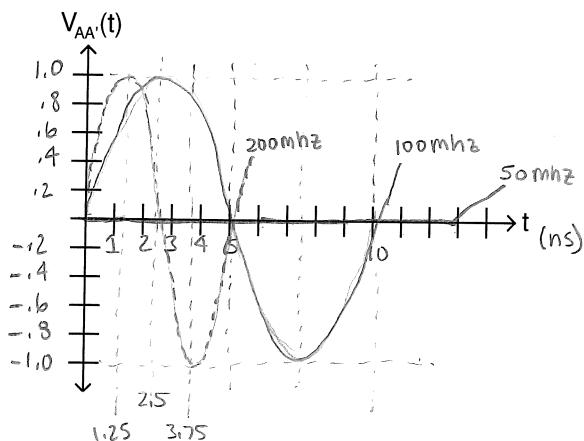


6. For the circuit below,

- (a) Sketch the voltage waveform at the input to the transmission line AA' for $f = 100\text{Mhz}$, $f = 200\text{Mhz}$, $f = 50\text{Mhz}$. Provide the units and scale on the graph.
- (b) For each frequency in (a), draw the value of $|V_{aa}(d)|$. The line is still 0.5λ long at 100Mhz.

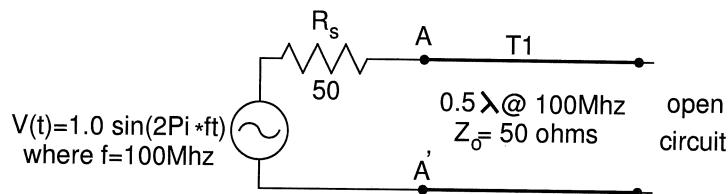

$\frac{\lambda}{2}$ line with open circuit end presents an open circuit to the input. At $2x$ the frequency its 1λ long, still reflecting the loss to the input. At $\frac{1}{2}$ frequency, the line is $\lambda/4$ long, presenting a short circuit to the input.