

8(a), (b)

```

Nov 28, 16 15:56 resonance.sp Page 1/1
Series and Parallel Resonant Circuits
*Uncomment the appropriate sections to alter the circuits
*and to view the results.

*series resonant circuit
*V_src vin gnd ac 1.0 sin ;1v ac source, no dc value
*r_src vin tie1 1.0 ;1 ohm resistor to sense current
*c_net tie1 tie2 2nf ;2nf network cap
*r_cap tie1 tie2 10Meg ;10Meg ohm resistor, models capacitor leakage
*l_net tie2 tie3 1uH ;1uh network inductor
*r_ind tie3 gnd 0.6 ;0.6 ohm, models inductor resistance

*parallel resonant circuit
V_src vin gnd ac 1.0 sin ;1v ac source, no dc value
r_src vin tie1 10k ;10k ohm resistor to sense voltage
r_cap tie1 gnd 10Meg ;10Meg ohm resistor, models capacitor leakage
c_net tie1 gnd 500pf ;500pf network cap
l_net tie1 tie2 2.5uH ;2.5uh network inductor
r_ind tie2 gnd 0.6 ;0.6 ohm, models inductor resistance

*T-line parallel resonator
*V_src vin gnd ac 1.0 sin ;1v ac source, no dc value
*r_src vin tl_in 10k ;10k ohm resistor to sense voltage
*t_line tl_in gnd tie1 tie1 z0=50 F=5Meg NL=.25 ; tline resonator
*r_dummy tie1 gnd 1G ;required DC path to ground for spice

.control
set hcopydevtype=postscript
set hcopypscolor=0
set color0=rgb:f/f/e
set color1=rgb:0/0/0
ac lin 1000 1m 10Meg

*parallel circuit measurments
plot vm(tie1) vm(vin, tie1) ;V across and relative I through resonator
hardcopy parallel_circuit.ps vm(tie1) vm(vin, tie1)

*series circuit measurments
*plot vm(tie1) vm(vin, tie1) ;V across and relative I through resonator
*hardcopy series_circuit.ps vm(tie1) vm(vin, tie1)

*T-line circuit measurments
*plot vm(tl_in) vm(vin, tl_in) ;V across and relative I through resonator
*hardcopy tline_resonator.ps vm(tie1) vm(vin, tie1)

.endc
.end


```

This file is downloadable from:

http://www.ece.orst.edu/~traylor/ece391/new.hw/quarter_half_behavior/solutions/resonator.sp

To run: `invoce ngspice, within ngspice`
`> source resonator.sp`


parallel resonant ckt.

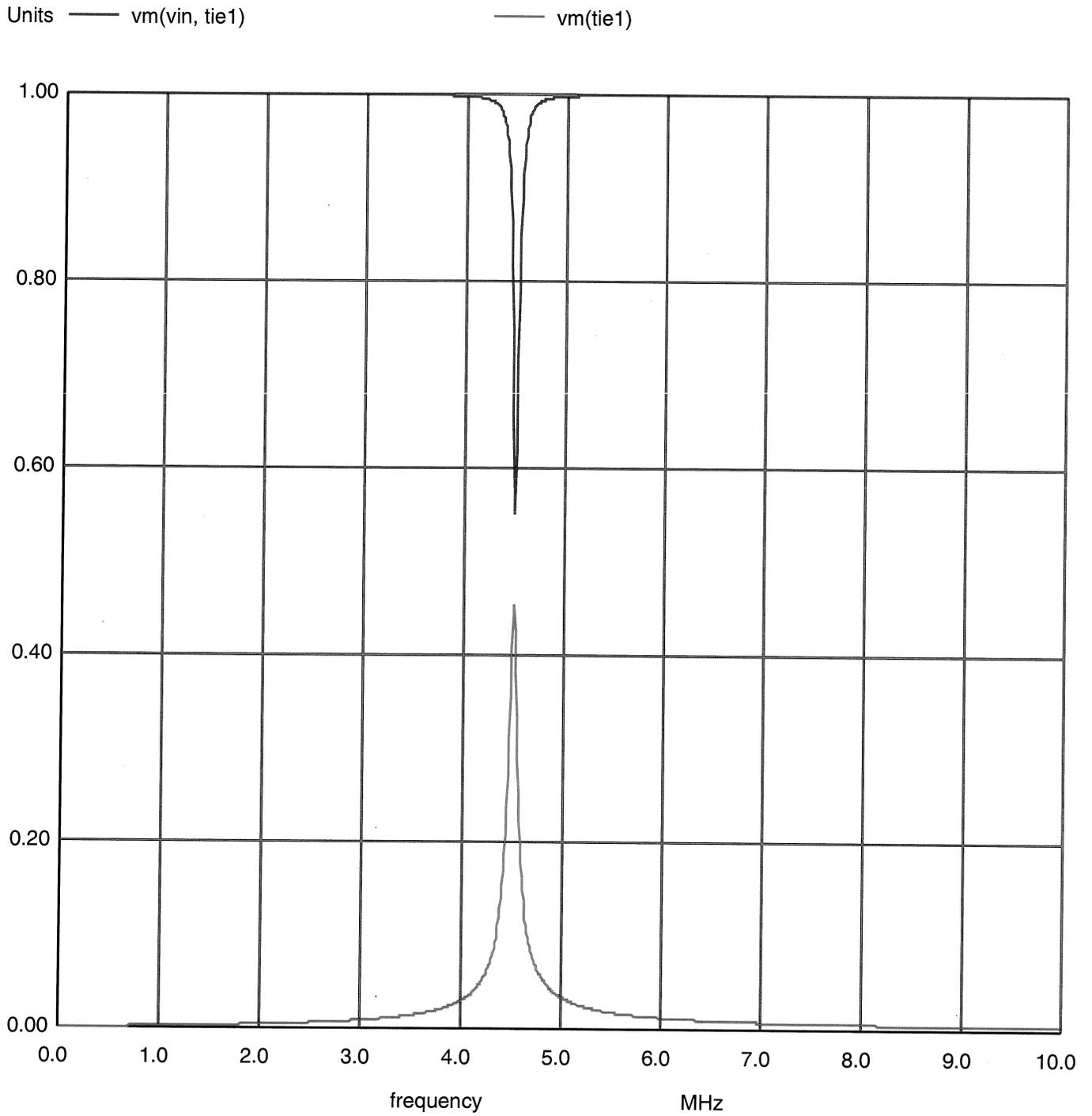

series resonant ckt.

Units — vm(vin, tie1)


— vm(tie1)

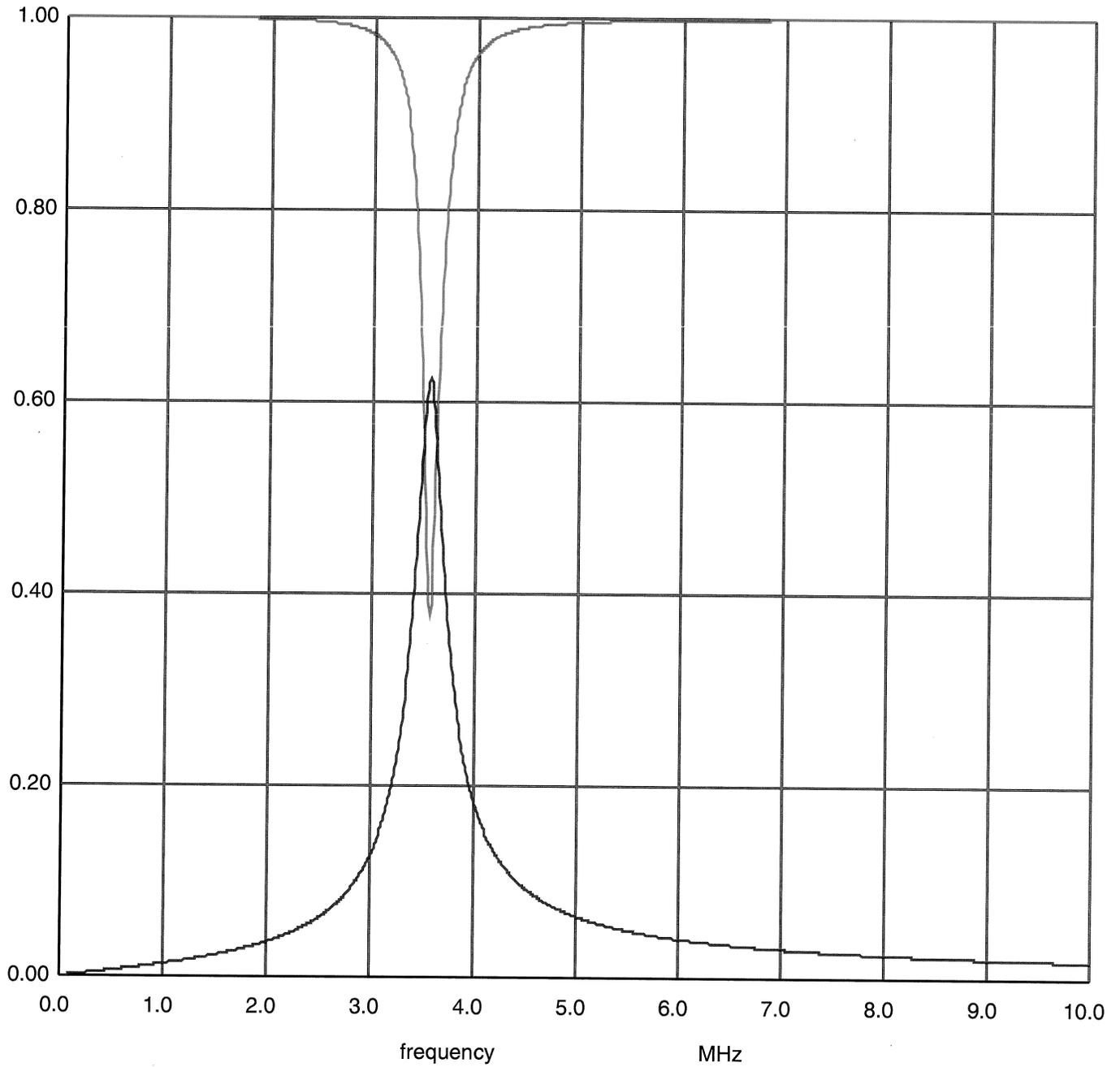

8(b)

4/5

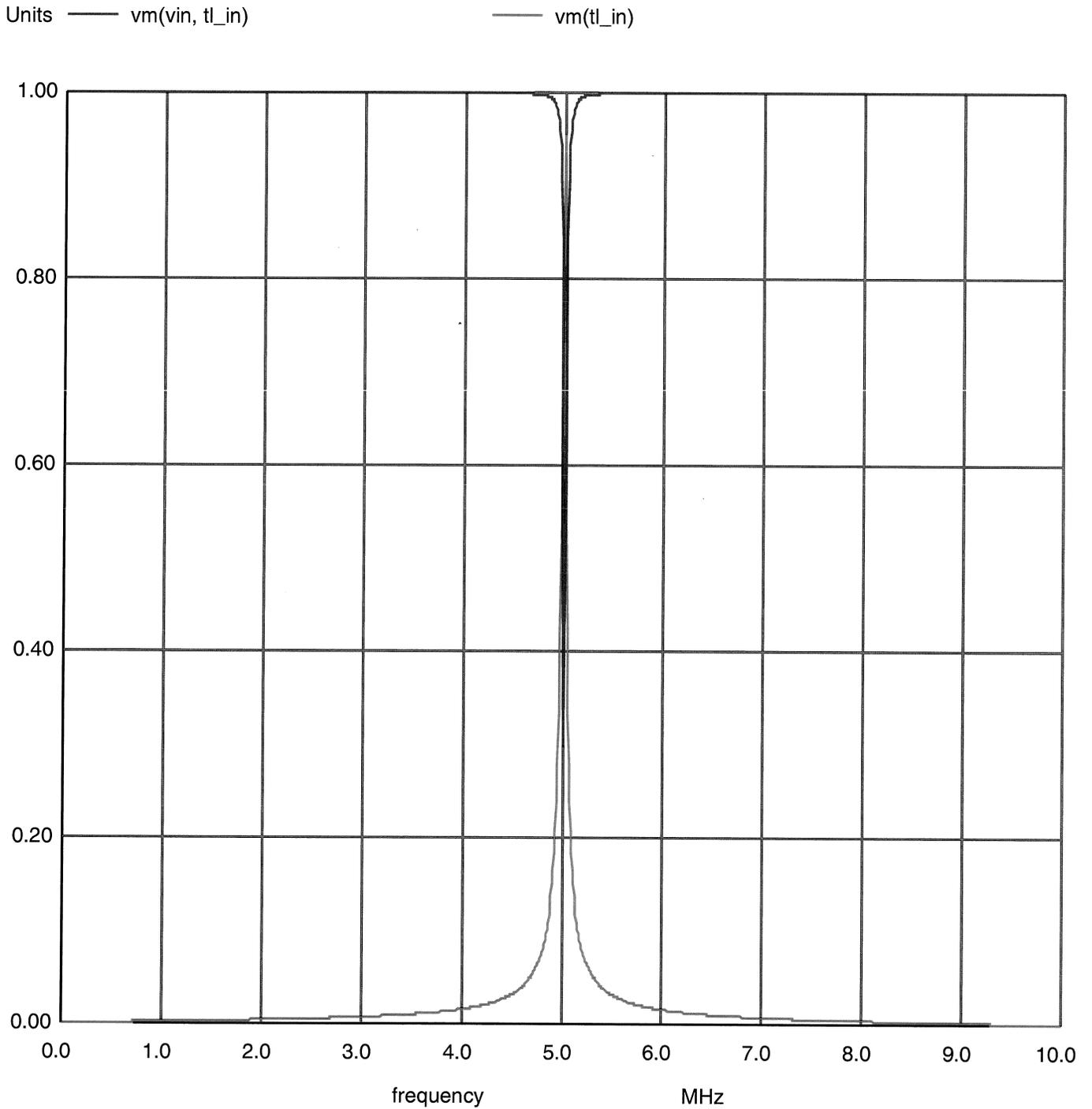+line resonator (looks like parallel resonator)
8(d)



parallel resonant ckt w 1.6Ω resistor
in series with the inductor

