

6.

(a) What are the voltage and current amplitudes of the first outgoing wave?

$$V_{o,1} = \boxed{5V}$$

$$i_{o,1} = V_{o,1} / Z_0 = \boxed{100mA}$$

(b) Determine the generator voltage, V_G .

$$V_G = 2 V_{o,1} \quad (\text{since } R_G = Z_0)$$

$$= \boxed{10V}$$


(c) Determine distance d at which the cable is damaged.

$$2t_0 = 6\mu\text{sec} = \frac{2d}{V_p} \quad (\text{roundtrip time})$$

$$\Rightarrow d = 3\mu\text{sec} \cdot V_p = 3\mu\text{sec} \cdot 200 \frac{\text{m}}{\mu\text{sec}} = \boxed{600\text{m}}$$

(d) Determine the voltage of the returning wave (reflected at the damaged location).

$$V_{o,1} + V_{r,1} = 8V$$
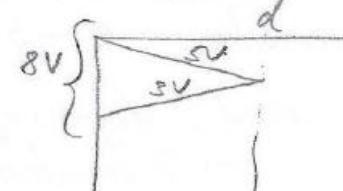
$$\Rightarrow V_{r,1} = 8V - 5V = 3V$$



(e) What is the reflection coefficient at the location of the damaged cable?

$$S = \frac{3V}{5V} = \boxed{0.6}$$

(f) How would you model the damaged section of the cable?

→ series resistance (since $S > 0$)

(other networks are also possible since we only know how much is reflected but not how much is transmitted)



$$S = 0.6 \quad \frac{R_L - Z_0}{R_L + Z_0} = 0.6 \Rightarrow R_L = Z_0 \frac{1+0.6}{1-0.6} = 50\Omega \frac{1.6}{0.4} = 200\Omega$$

$$R_L = R_s + Z_0 \Rightarrow \boxed{R_s = 150\Omega}$$