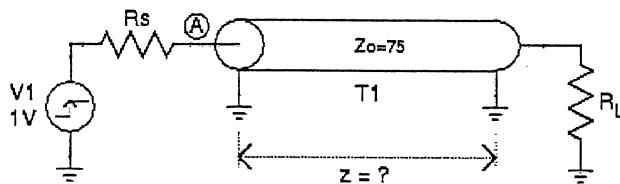


9. Consider the circuit and spice waveform for point "A" below. The generator launches the rising edge at 5ns. Find:

(a) The length z of the coax cable. $z = \underline{5 \text{ ns}}$

(b) $R_s = \underline{40 \Omega}$

(c) $R_L = \underline{10 \Omega}$




$$R_s: V_{in} = 1 \cdot \frac{75}{75+R_s}$$

$$1.65217 = \frac{75}{75+R_s}$$

$$1.65217(R_s + 75) = 75$$

$$1.65217R_s + 48.91 = 75$$

$$\underline{R_s = 40 \Omega}$$

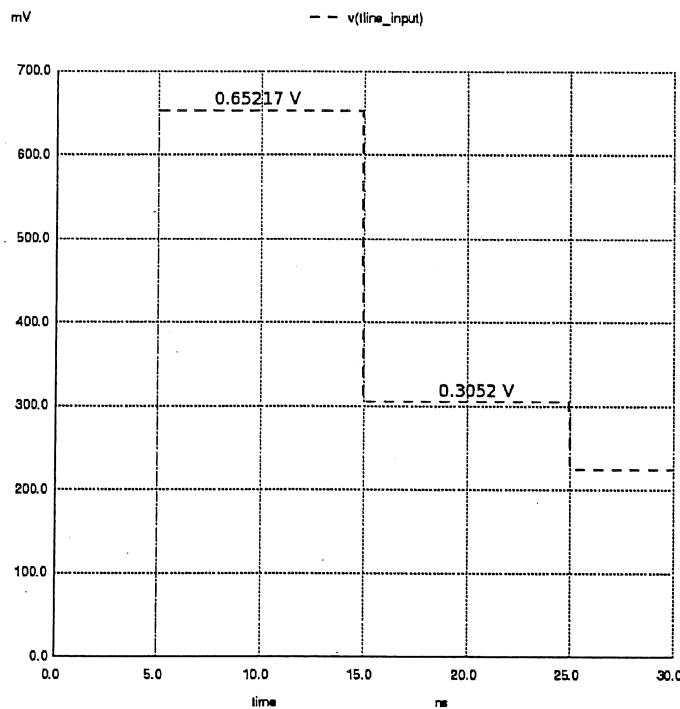

$$R_L: 3052 = 0.65217 + V_i^- + V_2^+ ; V_2^+ \text{ is } V_i^- \cdot P_s \Rightarrow P_s = \frac{40-75}{40+75} = -0.3043$$

$$3052 = 0.65217 + V_i^- (1 + P_s)$$

$$3052 = 0.65217 + V_i^- (1 - 0.3043)$$

$$-0.347 = 0.6957 V_i^-$$

$$V_i^- = -0.4988 \text{ And we know } P_L = \frac{V_i^-}{V_i^+}, \text{ so } P_L = \frac{-0.4988}{1.65217} = -0.7648$$

$$\text{Since } P_L \text{ is also } = \frac{R_L - 75}{R_L + 75}; -0.7648 = \frac{R_L - 75}{R_L + 75}$$

$$= 0.7648(R_L + 75) = R_L - 75$$

$$-0.7648 R_L - 57.36 = R_L - 75$$

$$-1.7648 R_L = -75 + 57 \Rightarrow \underline{R_L = 10.2 \Omega}$$