
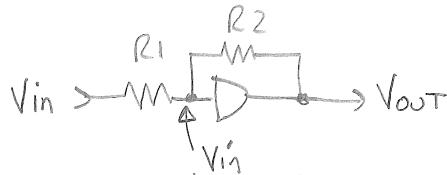


8. The Schmitt-trigger circuit:

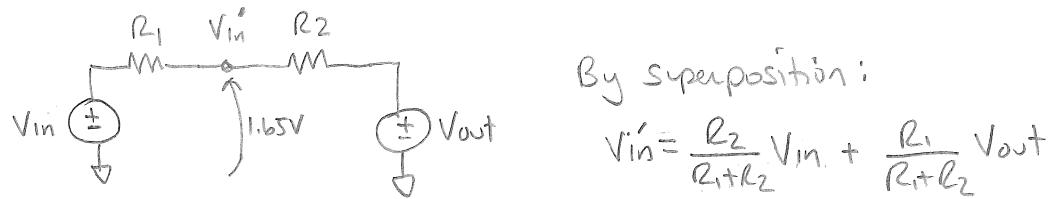

Since the output resistance of the buffer is zero ohms and its input resistance is roughly ∞ , it's obvious that the $5k\Omega$ input constraint is met when $R_1 + R_2 = 5000$.

In the condition where the output is 3.3V and the input voltage has just reached the lower threshold, we have:



With our constraint of $R_1 + R_2 = 5000$ and the given thresholds, for the case where the input has fallen to the lower threshold we have:

$$1.65 = \left(\frac{R_2}{5000}\right) 1.25 + \left(\frac{R_1}{5000}\right) 3.3$$

$$(A) 8250 = 1.25R_2 + 3.3R_1$$

In the other case where the input has just risen to the upper threshold:

$$1.65 = \frac{R_2}{5000} (2.05) + 0$$

$$\text{thus } R_2 = \underline{\underline{4020 \Omega}}$$

Solving for R_1 using (A):

$$8250 = 1.25(4020) + 3.3R_1$$

$$\underline{\underline{R_1 = 977 \Omega}}$$

Our circuit is thus: $V_{in} \xrightarrow[977]{\quad} \text{Op-Amp} \xrightarrow{4020} V_{out}$

