

The Lattice (or Reflection) Diagram

The Lattice diagram provides a graphical bookkeeping method to keep track of reflections from both near and far ends of a T-line.

It can also be used when multiple T-lines of different Z_0 are in series.

It shows the impedance boundaries

reflection coefficients at each end


flight time

voltage and current at any point (z out) on the line

cumulative voltage at both ends of the line

A voltage or current waveform versus time plot can be made from the Lattice diagram

The Lattice Diagram



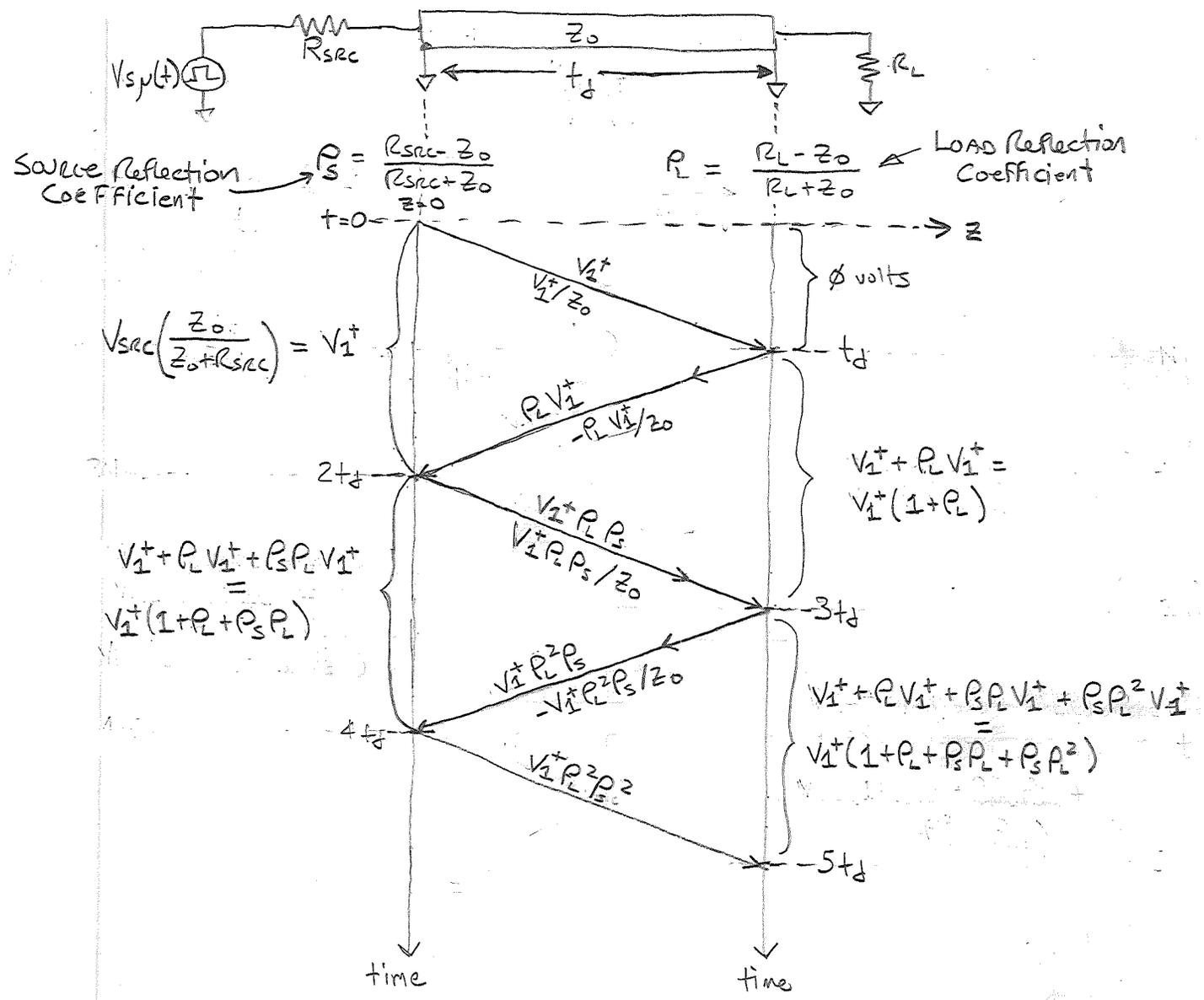


The eventual cumulative voltage at each end of the T-Line converges to:

$$V_{\infty} = V_{src} \left(\frac{R_L}{R_L + R_S} \right)$$


Lattice Diagram - single driver/receiver, source termination too big

$(P_s > 0, P_L > 0)$

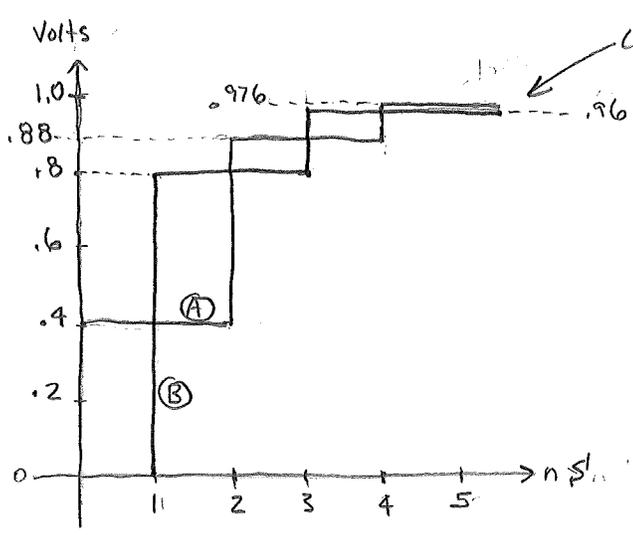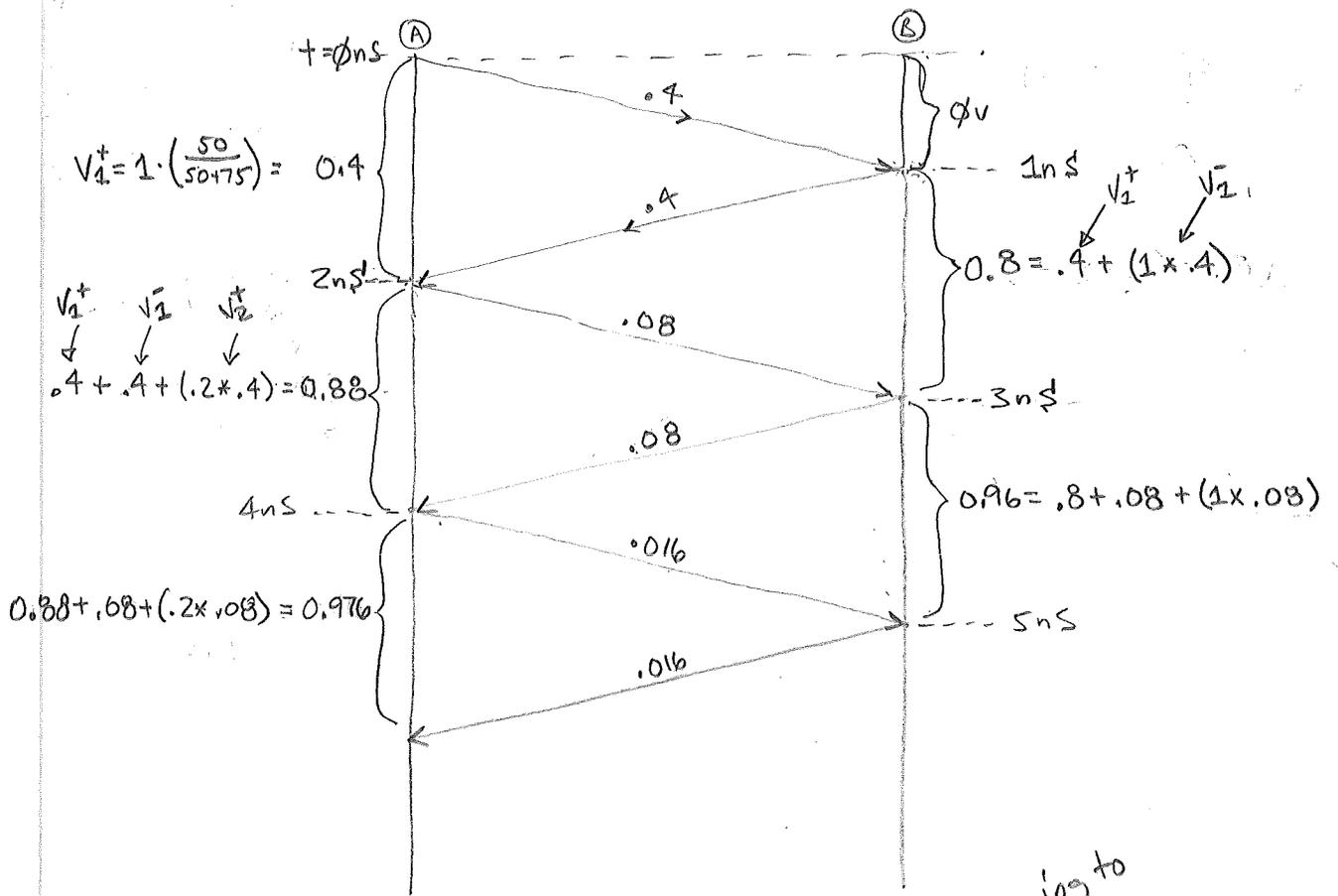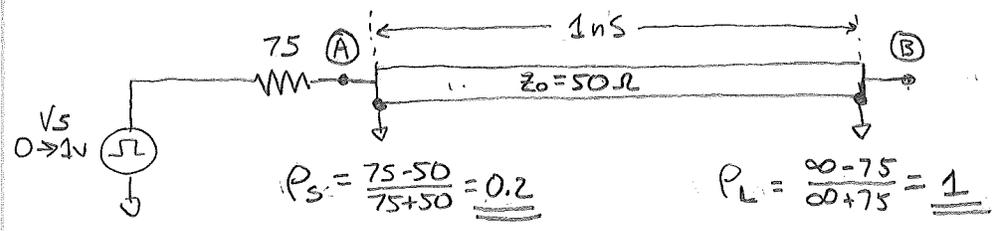


converging to $V_s = 1V$
 source termination is too big!
 excessive delay



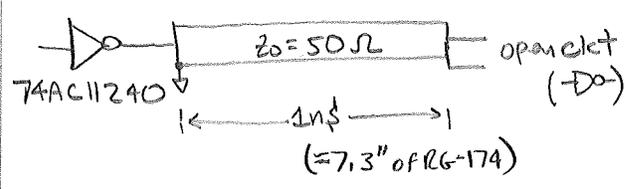
Lattice Diagram - single driver/receiver, source termination too small






74AC11240 equivalent to:

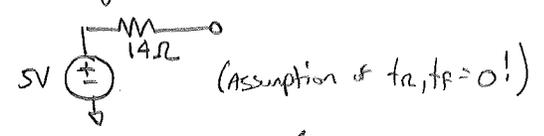

equivalent ckt:

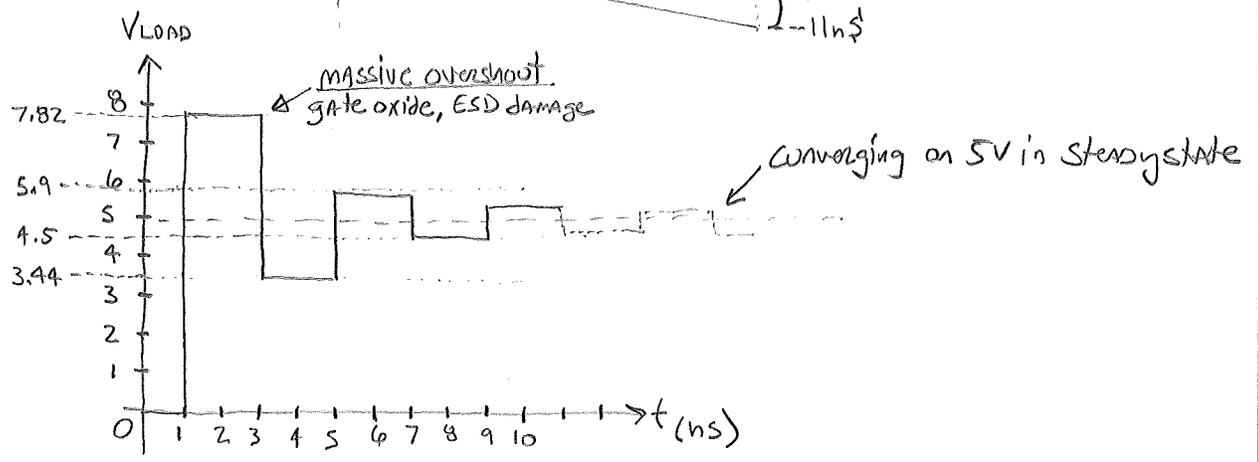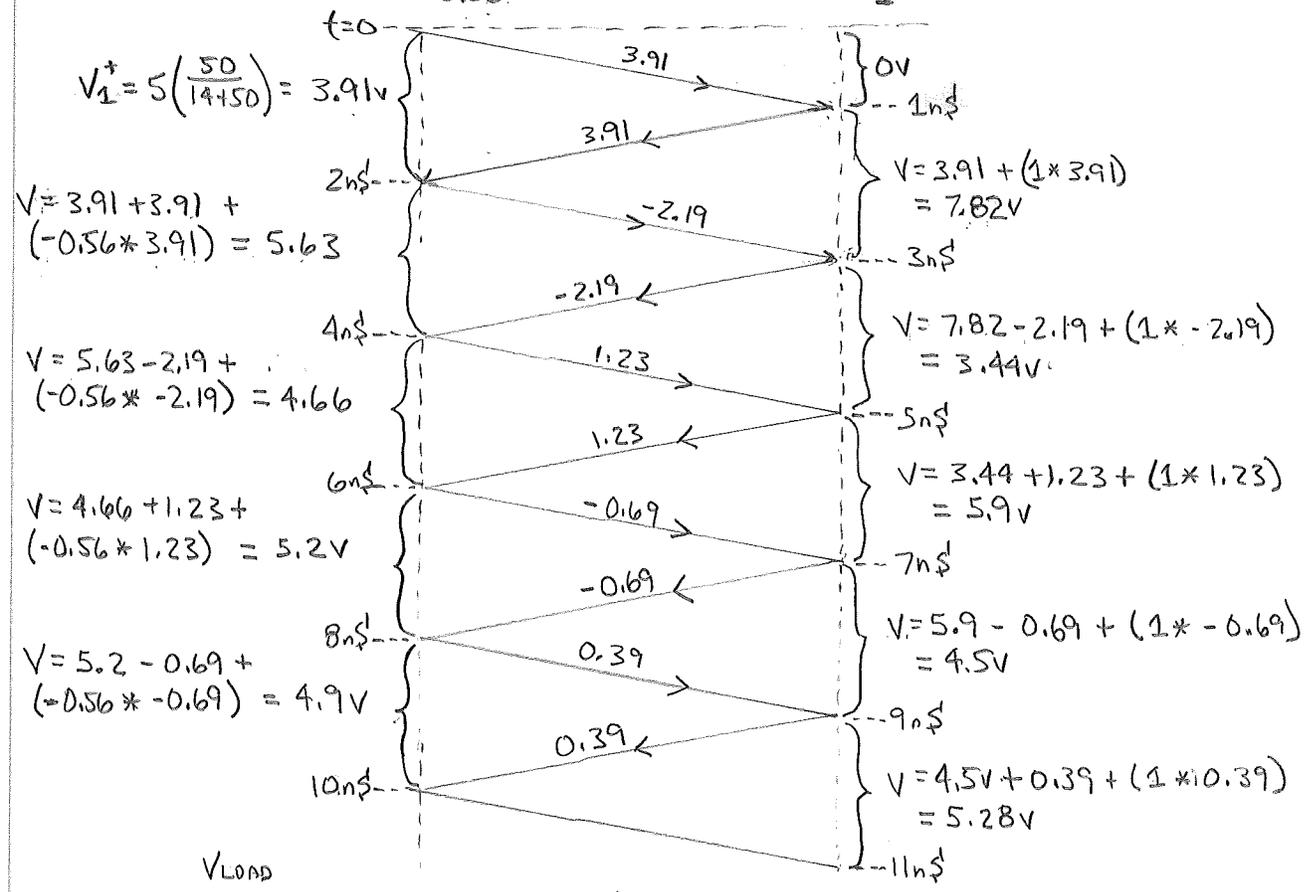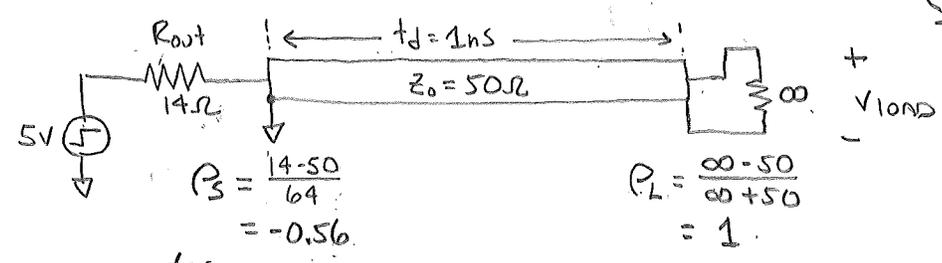

($P_{src} > 0, P_{load} < 0$)

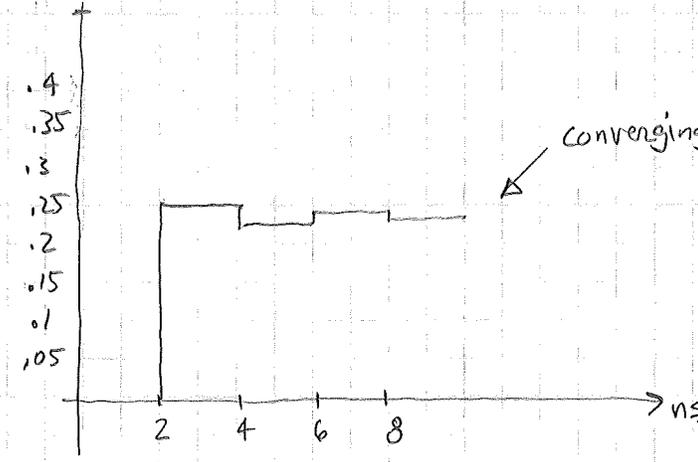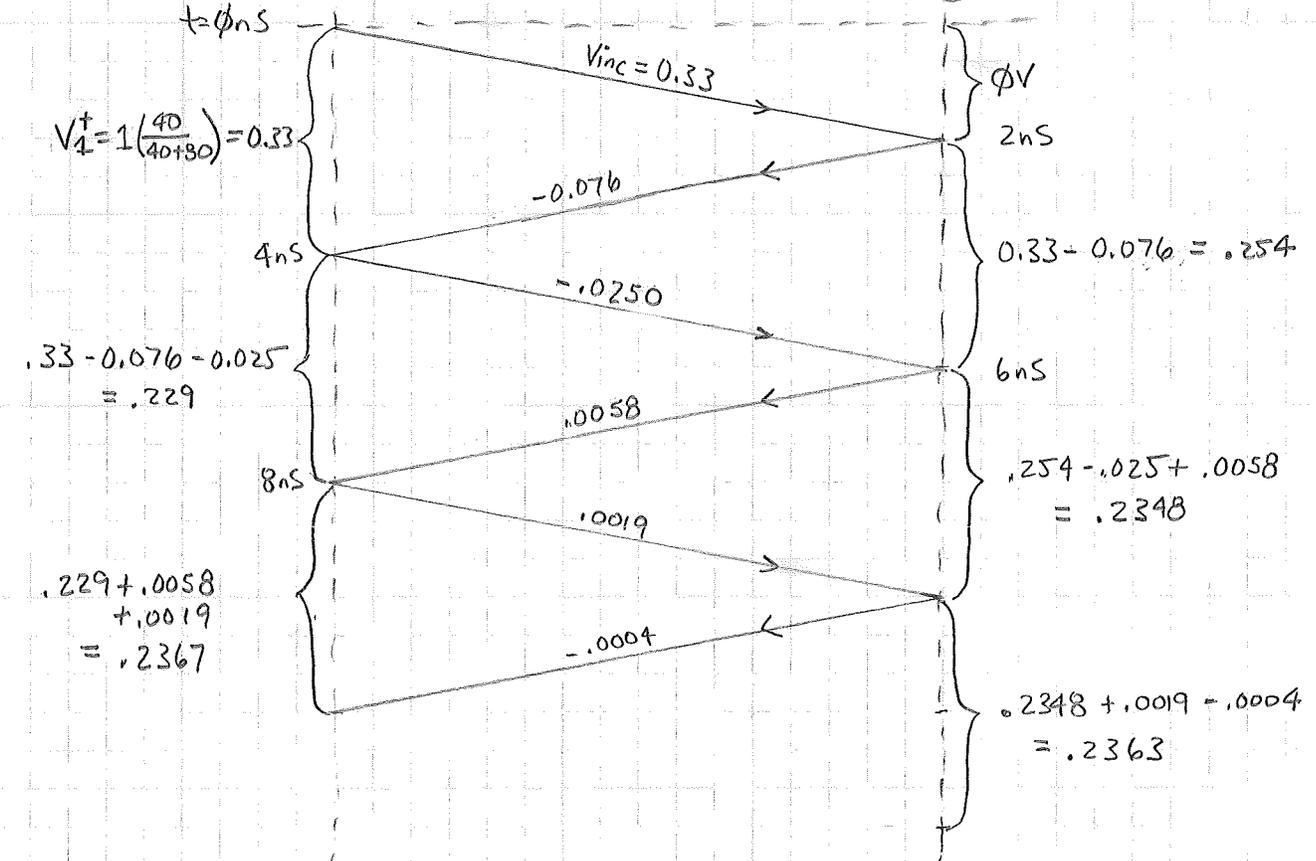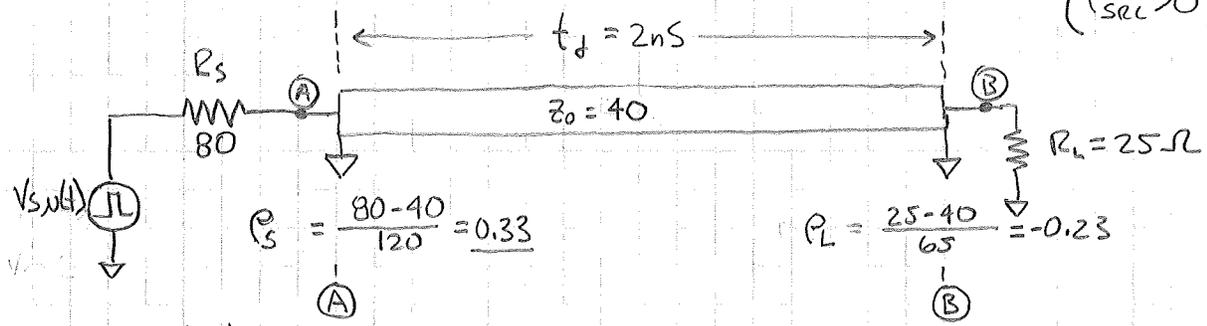

converging to: $V_s \left(\frac{R_L}{R_L + R_S} \right) = \frac{25}{25 + 80} = 0.2381 V$