

TRANSMISSION Lines - why is it important?

- The study of TRANSMISSION Lines (T-lines) is part of the larger field of Signal Integrity (SI)
- Signal Integrity consists of:
 - T-Lines: getting signals from source to destination while preserving their important characteristics,
 - Electromagnetic Interference (EMI): keeping other signals from effecting my signals and keeping my signals from effecting others. (minor focus)

• As An Engineer using T-lines, you want to be Able to:

- Launch A signal from source to destination AND

- do so in An acceptable time frame OR

- with An acceptable waveshape OR

- with A maximum power transfer to the load AND

- while not interfering with OR being interfered by other signals AND

- doing so with the given design constraints

You should be able to: (eventually!)

- Identify situations where conductor pairs behave as T-lines
- Be able to develop mathematical ^{Ans} OR circuit models of
 - T-lines
 - drivers, receivers
 - discontinuities (R, L, C, Z₀)
- Be able to design an interconnect that provides correct operation via
 - termination schemes
 - conductor topology
 - impedance matching
- Be able to confirm by simulation or computation that your solution works
 - spice, matlab, smith chart

T-lines, terminations, matching networks

ECE391 is focused on the design and use of electrical structures that deliver electrical waveforms to electrically distant loads.

I, V, P

edge rate, wavelength
component size

Some definitions + terminology


• Signals

- digital ("1" or "0") voltage waveforms 
- Analog (continuous) voltage and current waveforms 

• "Driver"


- A driver is the entity that "launches" or signal
- A digital driver is usually a CMOS inverter output regardless of gate type

- eg. 

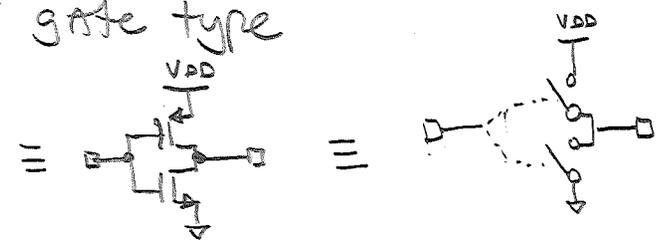

Characteristics:
 $Z_{in} \Rightarrow$ high
 $Z_{out} \Rightarrow$ low

spice model:

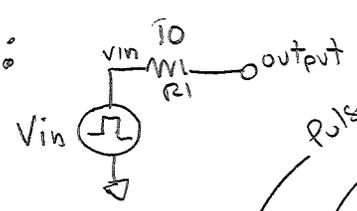

netlist

```

Vin vin 0 Pulse(0 1.0 2n 1n 1n 40n 80n)
R1 vin output 10

```


Pulses to IV
 2ns delay
 1ns tr
 1ns tf
 pulsewidth
 period



Some definitions + terminology

• Driver (cont.)

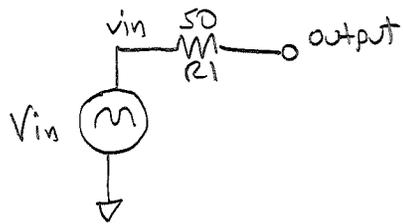- A analog driver could be an analog amplifier, discrete or integrated
- An antenna ... it drives a T-line to a receiver
- A T-line ... it could drive another T-line or low noise amplifier
- Spice model of a 50Ω output resistance amplifier




netlist
 Vin vin ϕ AC (sin ϕ 1.0 29.6m)
 R1 vin output 50

type of waveform
 DC offset
 Amplitude V_{PP}
 frequency

Some Definitions + Terminology

• Receiver

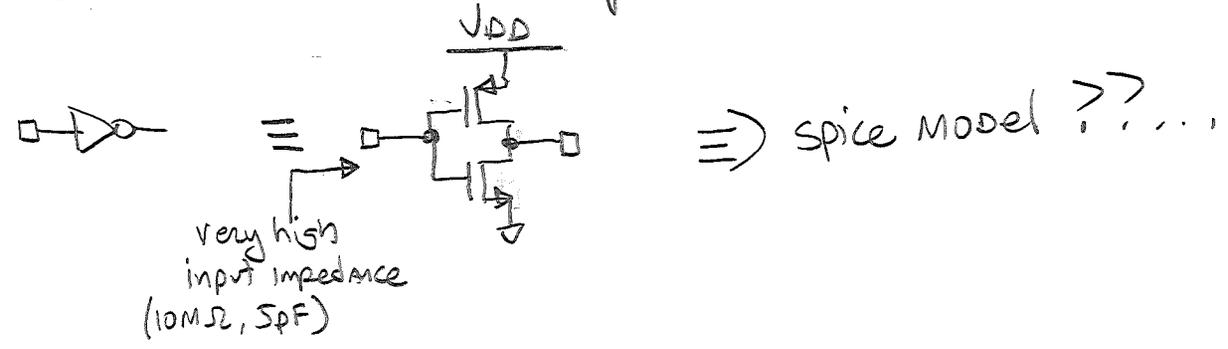
- A receiver is where the launched signal is sensed (voltage, current, power)
- A digital receiver is usually a CMOS inverter



- An analog receiver could be a discrete or integrated amplifier typically exhibiting a specified input impedance that is mostly (but not always) resistive. => spice model?
- An analog receiver could also be an antenna or another T-line. => spice model?

- Analog receiver (cont)

- Could be a resistor "—M—"

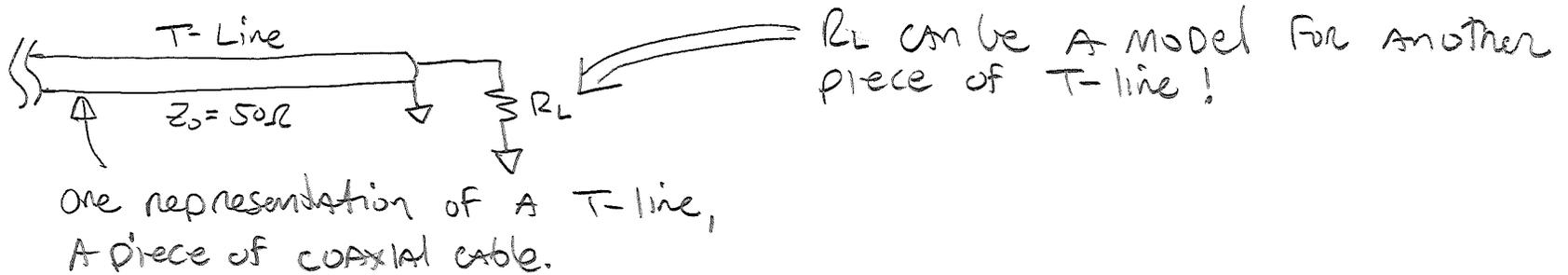

Why would you want to do this?!


Although we sometimes model T-lines as a resistive load, they DO NOT exhibit a DC resistance equal to their stated impedance.

In other words, a 50Ω coax cable does not exhibit a 50Ω DC resistance. Likewise, a T-line may exhibit an "apparent impedance of "X" ohms, ^{but} it does not dissipate any power for lossless lines.

Some definitions + terminology


"lightly loaded", "heavily loaded"

- consider

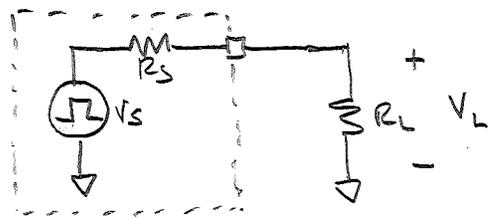

What R_L makes V_L begin to approach V_s ?

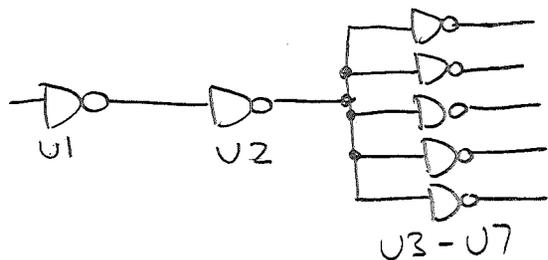Ans: An R_L that "lightly loads" the Thevenin source



$U1$ is lightly loaded

$U2$ is heavily loaded

Definitions + Terminology (cont)

Switching Threshold - the voltage level at which a digital logic gate decides if an input is logic "1" or "0".

- usually about $V_{DD}/2$
- guaranteed levels :
logic 1 $\geq 0.7V_{DD}$
logic 0 $\leq 0.3V_{DD}$

Termination - typically, a resistor placed at the driver or receiver. The resistor helps create the conditions for the proper operation of a T-line.


- can also be a diode, inductor, capacitor, an active device or even another T-line.

"Looking Into" - An anthropomorphism that describes the "apparent impedance" experienced by a incoming or outgoing wavefront.

Definitions + Terminology


- "ringing"

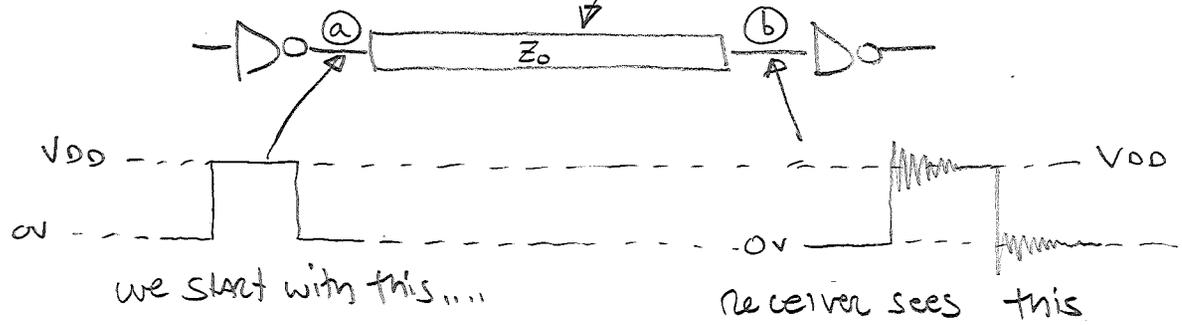Another Representation
of a T-line... Ground
return is understood.



"ringing" is the dampened sinusoid at the edges of signals that oscillates around the supply rails

- "overshoot", "undershoot"


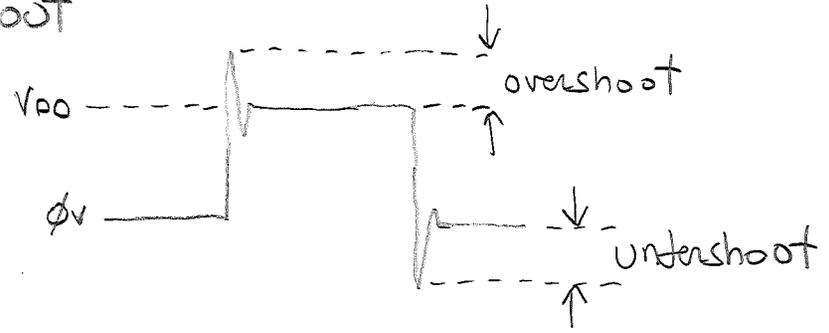


Problems caused by T-line phenomena

Ringing can be a source of EMI at unexpected frequencies

Mis-terminated T-lines often "ring" especially with fast edges.
(or line length)

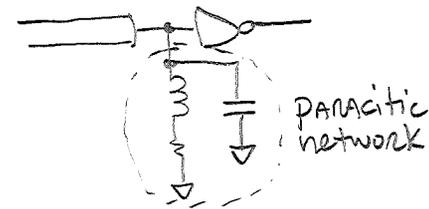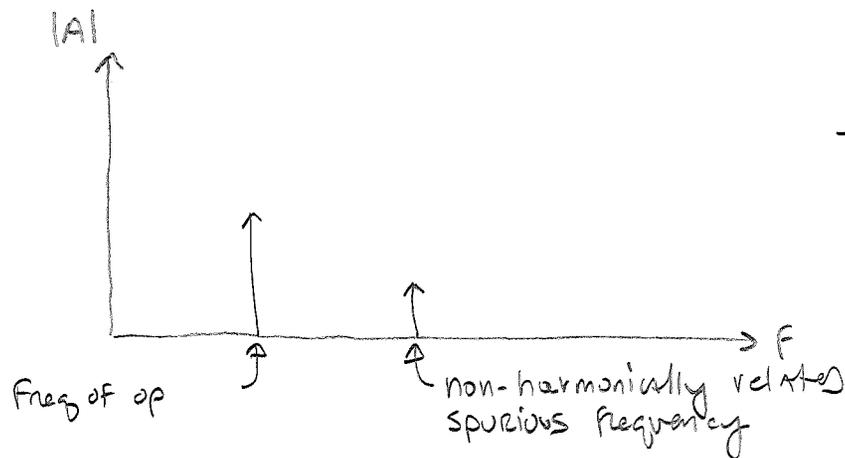The ringing frequency depends on parasitic $L+C$ and is not necessarily related to the driving frequency.





Problems caused by T-line phenomena.

Reliability Issues with Overshoot / Undershoot

CMOS Input:

$Z_0 = 50\Omega$

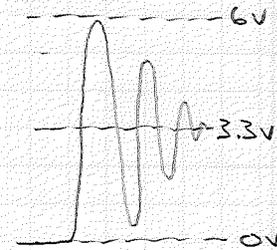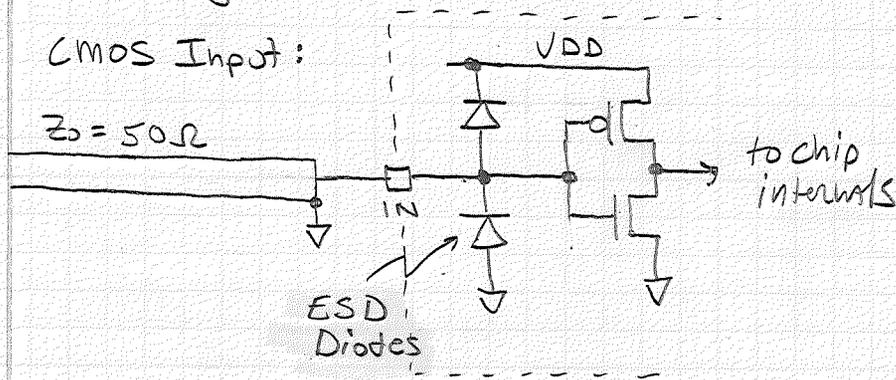


ESD diodes are very fast, very small diodes. EASILY DAMAGED.

Driven repeatedly from a 50Ω or less source will quickly kill them.


Another Problem

Timing Issues

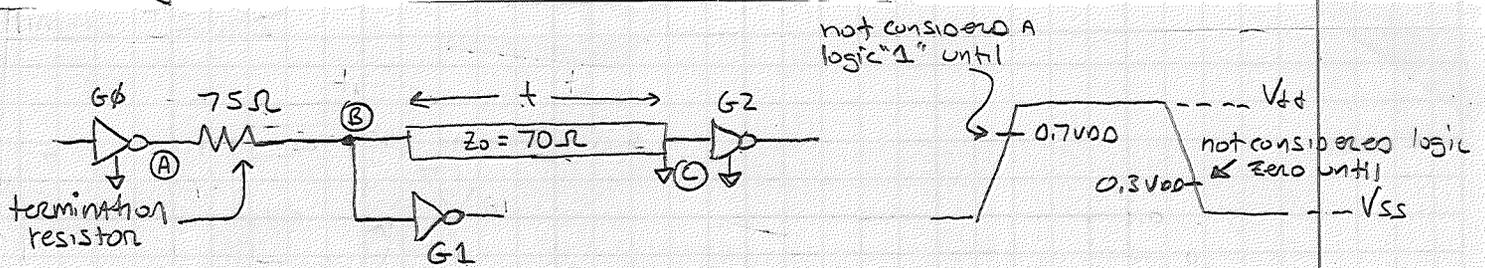


IF the switching threshold of G_0, G_1, G_2 are $0.7V_{DD} + 0.3V_{DD}$
 For guaranteed $V_{IH} + V_{IL}$, who switches first, G_1 or G_2 ?

G_2 switches first!

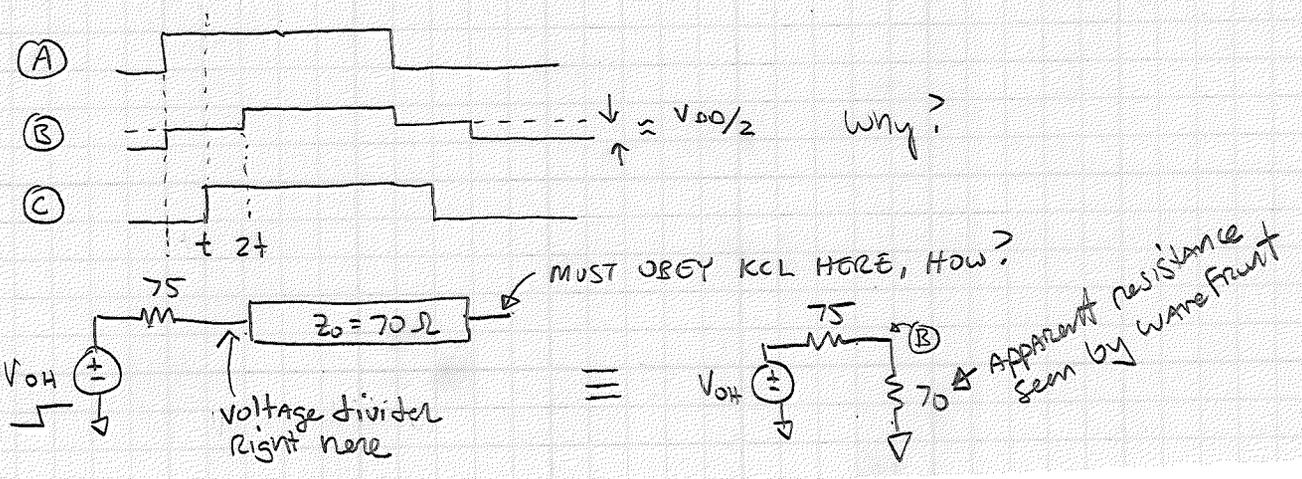


More Problems

MAXIMUM POWER TRANSFER

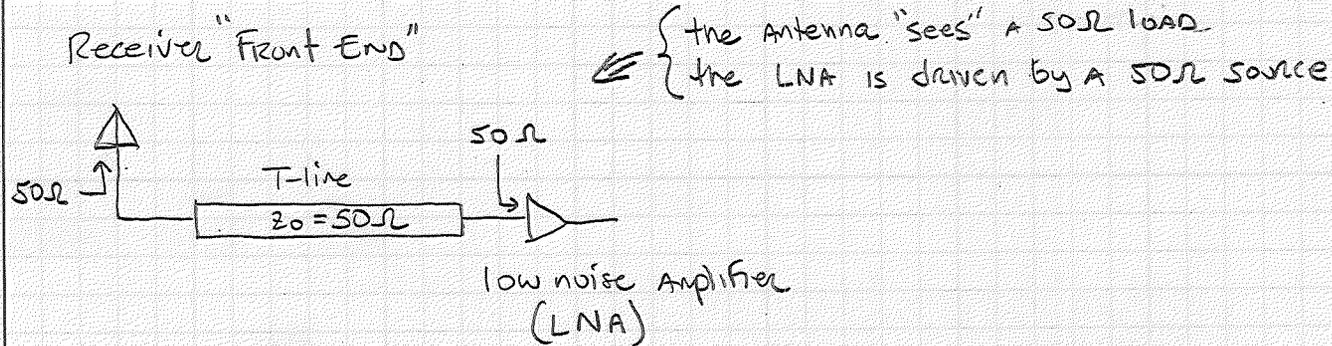

Antenna is the 50 Ω source. It is driving the LNA thru a T-line. For maximum power transfer the Antenna should "look into" a 50 Ω impedance.

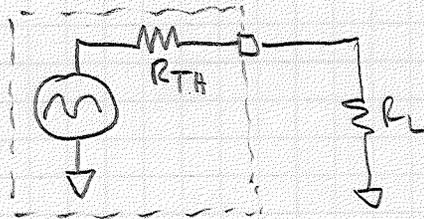
At the LNA, the T-line is the source and should present a 50 Ω driving point impedance to the LNA for max power xfr.



MAX power is delivered when $R_L = R_{TH}$

Special Uses of Transmission Lines

Impedance Transformation

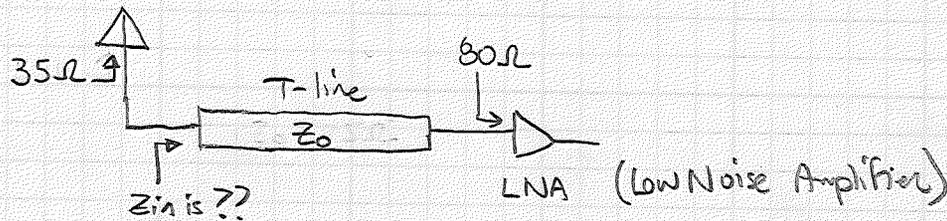

Depending on the T-line's electrical length and the frequency of operation, the antenna may or may not be "looking into" 80Ω . The apparent input impedance at the T-line may vary widely.


With continuous waveforms, depending on line length, frequency and line loss, a 50Ω coax may look like anything from 0Ω to $\infty\Omega$.

This is actually good news! We can transform impedances.

In steady state AC condition apparent impedance looking into a T-line is defined by the terminal V_{in}/I_{in} condition.


Special Uses Cont.

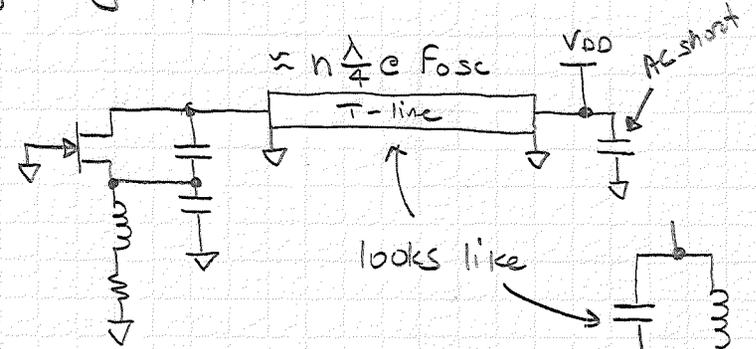• Under correct conditions, T-lines appear to be a very high quality LC resonator.




- self shielding
- mechanically very stable
- very high Q factor

looks like

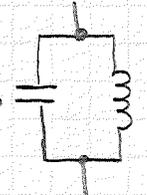

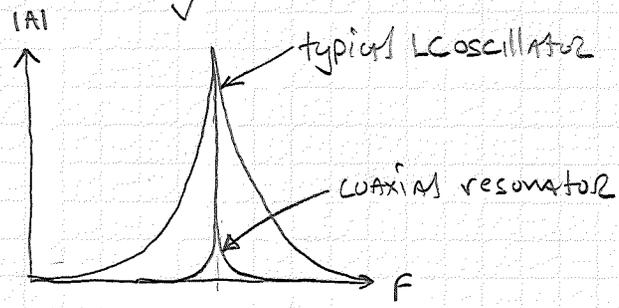
$f_{res} = \frac{1}{2\pi\sqrt{LC}}$ what is Z



- At multiples of $\frac{\lambda}{4}$, T-lines look like a pure inductor or capacitor.

- At $\frac{\lambda}{4}$ multiples, T-lines may also be used to transform impedances like a transformer


Transmission Line Examples

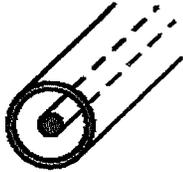


coaxial line




two-wire line (also twisted-pair)

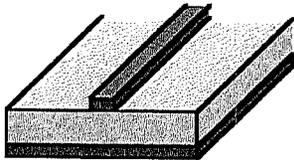


microstrip

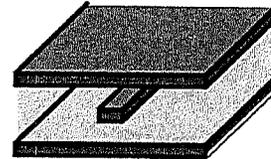

stripline

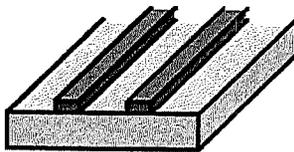

coplanar strip (CPS)

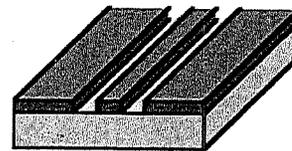

coplanar waveguide (CPW)

• A conductor pair is or is not a transmission line because of the:

- frequency or wavelength of the signal
- velocity of propagation on the line
- rise time of the signals (fall time too) on the line
- physical length of the line

not just the physical configuration.

("looking into" the 50Ω line, it also may not "look like" 50Ω!)

• A 50Ω coaxial line is not always a T-line.

• We want to know when we have a T-line scenario.